
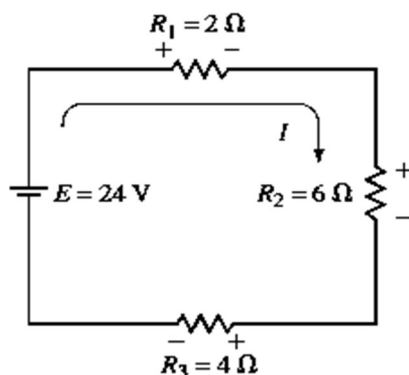


Review Exercise

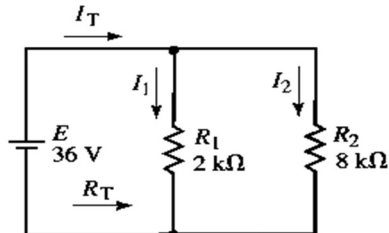- For the series circuit shown below, find the following quantities



- Total resistance, R_T
 - Circuit current, I .
 - Voltage across each resistor
 - Power dissipated by each resistor.
 - Power delivered to the circuit by the voltage source.
 - Verify that the power dissipated by the resistors is equal to the power delivered to the circuit by the voltage source.
- For the circuit of this figure, determine the following quantities:



- R_T , I_T
 - Power delivered by the voltage source
 - I_1 and I_2 using the current divider rule
 - Power dissipated by the resistors.
- find the total resistance R_T and conductance G_T for the circuit shown

