

Final Assessment of Electrical Workshop (Domestic Installation)

Question:

- A. Draw a circuit and wiring diagram for two lamps connected in parallel, controlled from two different positions, and one socket outlet.
 - B. List the tools, materials, and equipment required to install the drawn circuit.
-